

This is the simulation of Carry Look Ahead adder with the behavioural one. Here, the operation is similar to that of the carry look ahead adder. The difference is that we have designed it using partial full adders and look aheads. Here, we have not used any of them. Instead of them, we directly assigned the addition. In this one, we need to convert each of them into unsigned and then we need to do the addition which requires some extra circuit. This is not a synthesizable circuit.

